

2021/12/07

Project 2 – Cell-Based Layout Design

11010CS312000

Introduction of Integrated Circuit Design, NTHU

Outline


- Cell-Based Design
- Standard Cell Setting
- Cell Duplication for Logic Function
- Example
- Project
- Grading

Outline


- Cell-Based Design
- Standard Cell Setting
- Cell Duplication for Logic Function
- Example
- Project
- Grading

Cell-Based Design (1)


- Based on the idea of hierarchical design
- Do not care about the internal details at the cell-level design

 

NAND2

 


NOR2

 

INV

Cell-Based Design (2)

- Weinberger image array

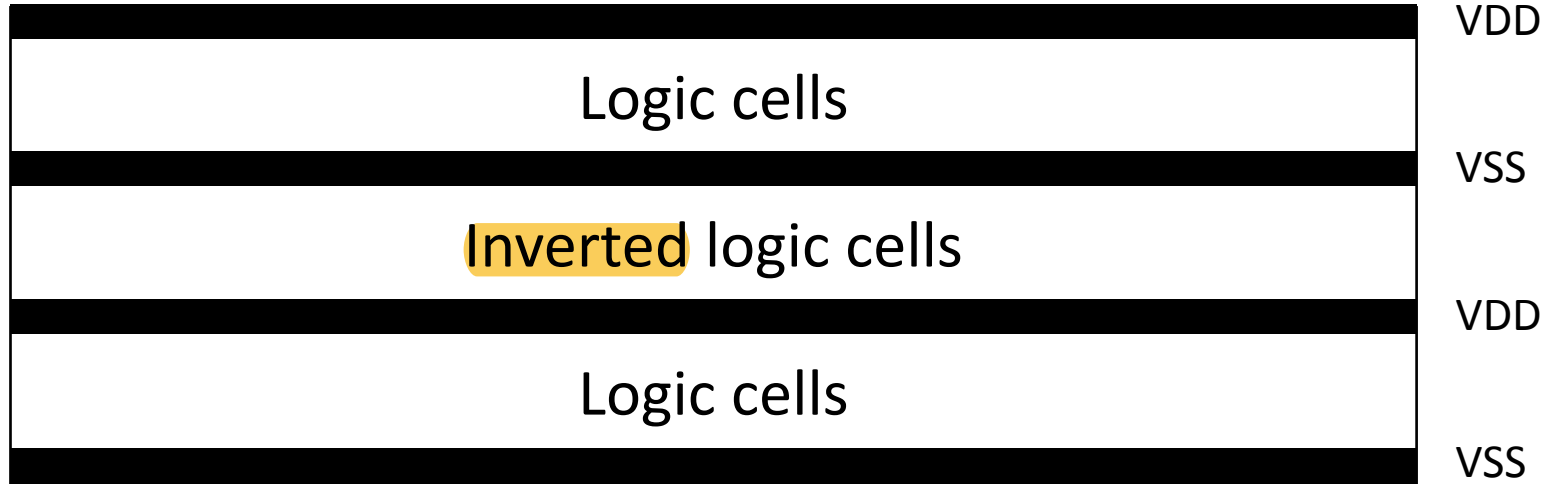

Outline

- Cell-Based Design
- **Standard Cell Setting**
- Cell Duplication for Logic Function
- Example
- Project
- Grading



Library Prepared

- Upload library “VLSI_LIB” to workstation
 - `~/layout/VLSI_LIB`
- You may use the same directory used in Project1 since the environment settings are still the same, i.e., DRC, LVS rule files, `calibre.csh` and `018.tf` etc. are also necessary.


```
[lhsiung21@ic28 ~/layout]$ ls
018.tf          CIC18_Calibre_DRC.drc  ic.csh          project2
calibre.csh     CIC18_Calibre_LVS.lvs  libManager.log  VLSI_LIB
cds.lib         display.drf            project1
```

New Project Library Creation

 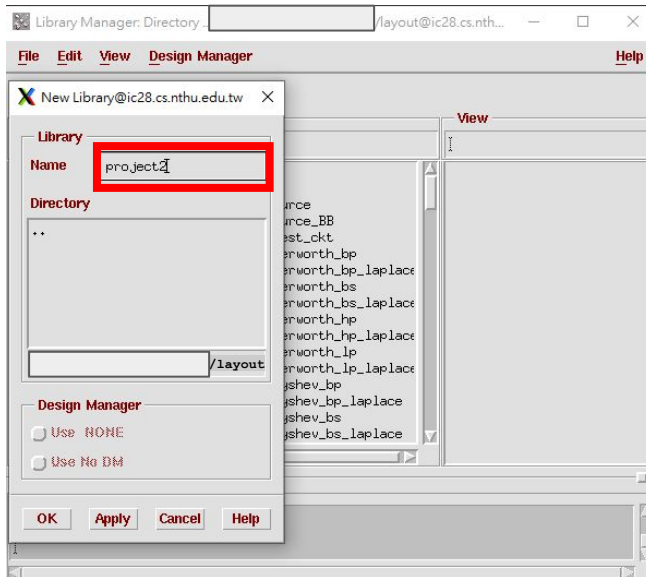
- Please refer the slides of Project1
 - Create a library named “project2”
 - Create a cell view named “FA”





Set Library Path (1)

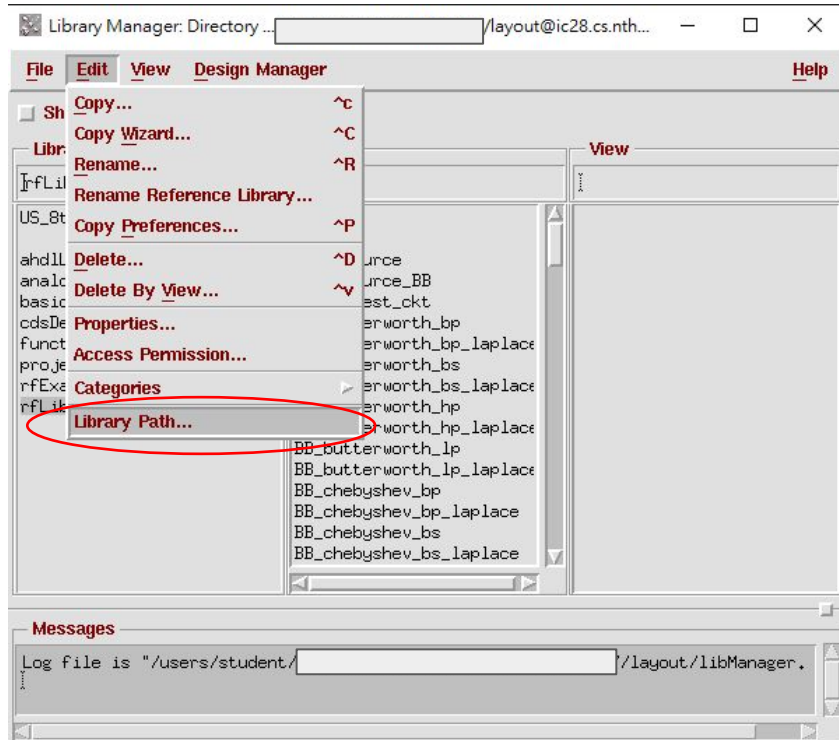


Set Library Path (2)

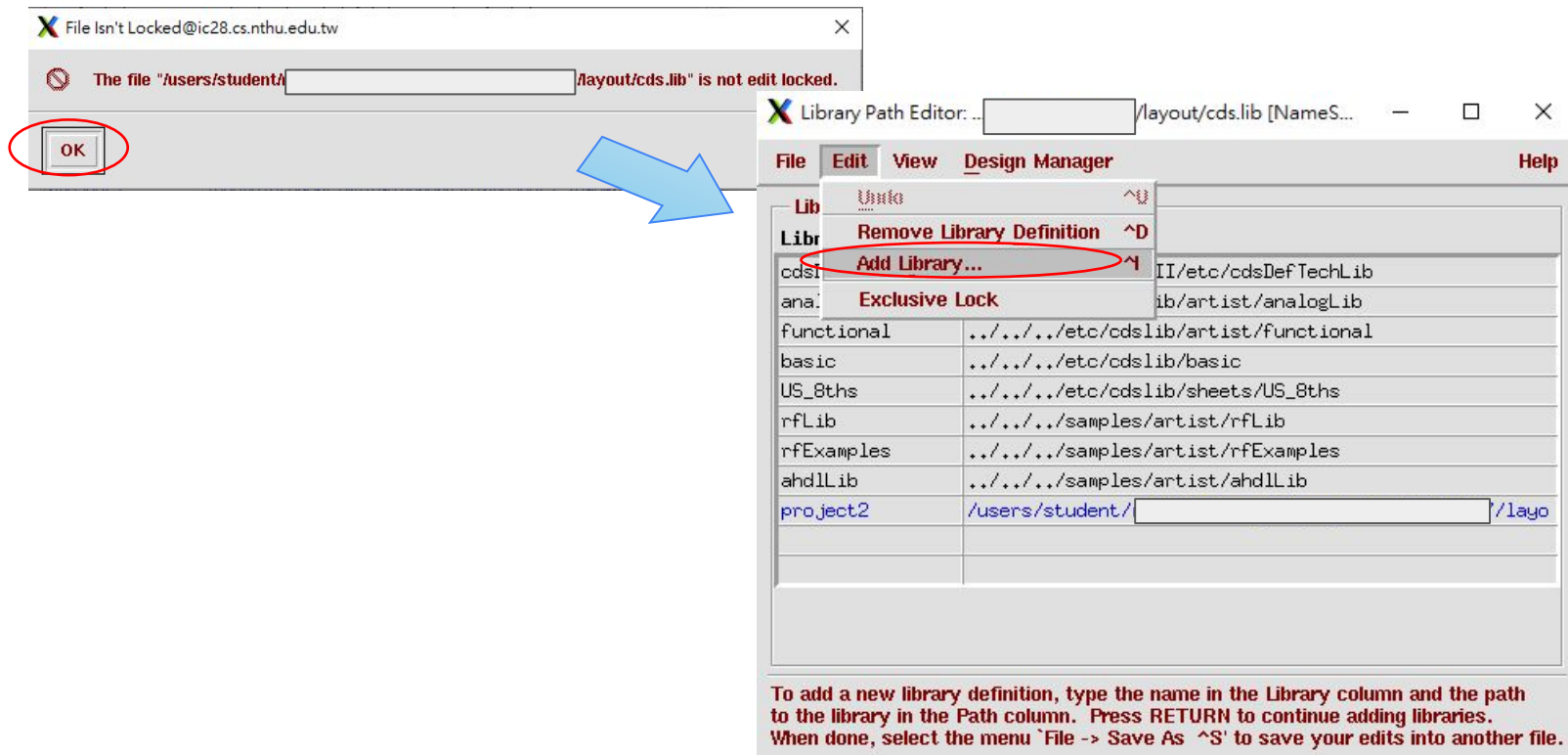


Set Library Path (3)

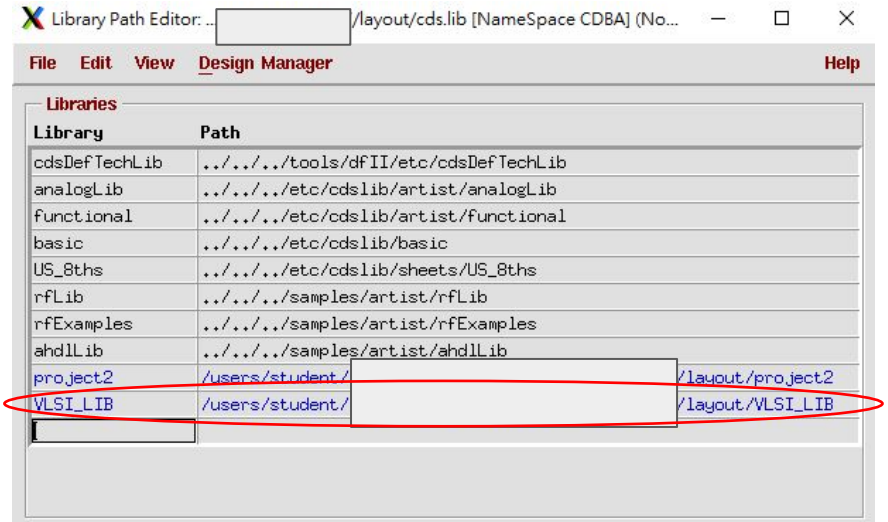 

Set Library Path (4)

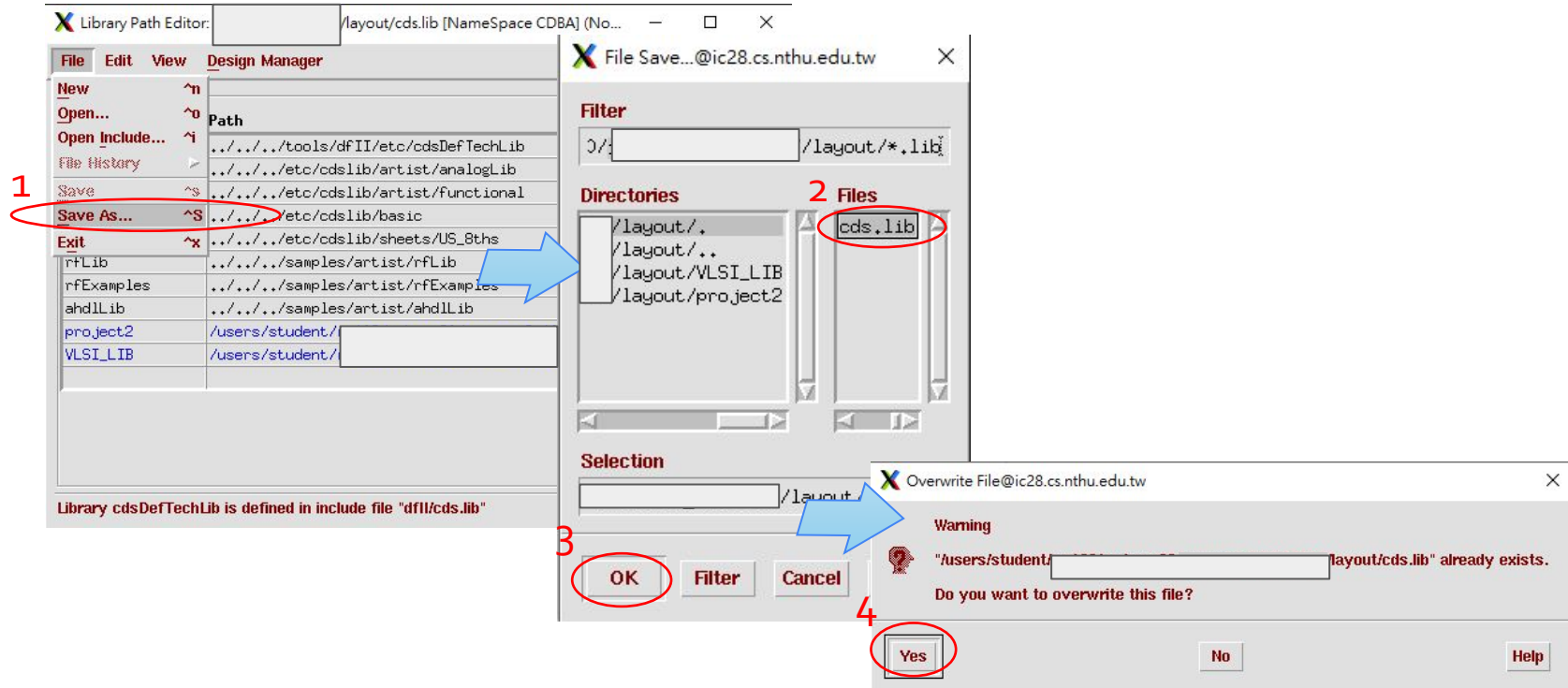


Set Library Path (5)

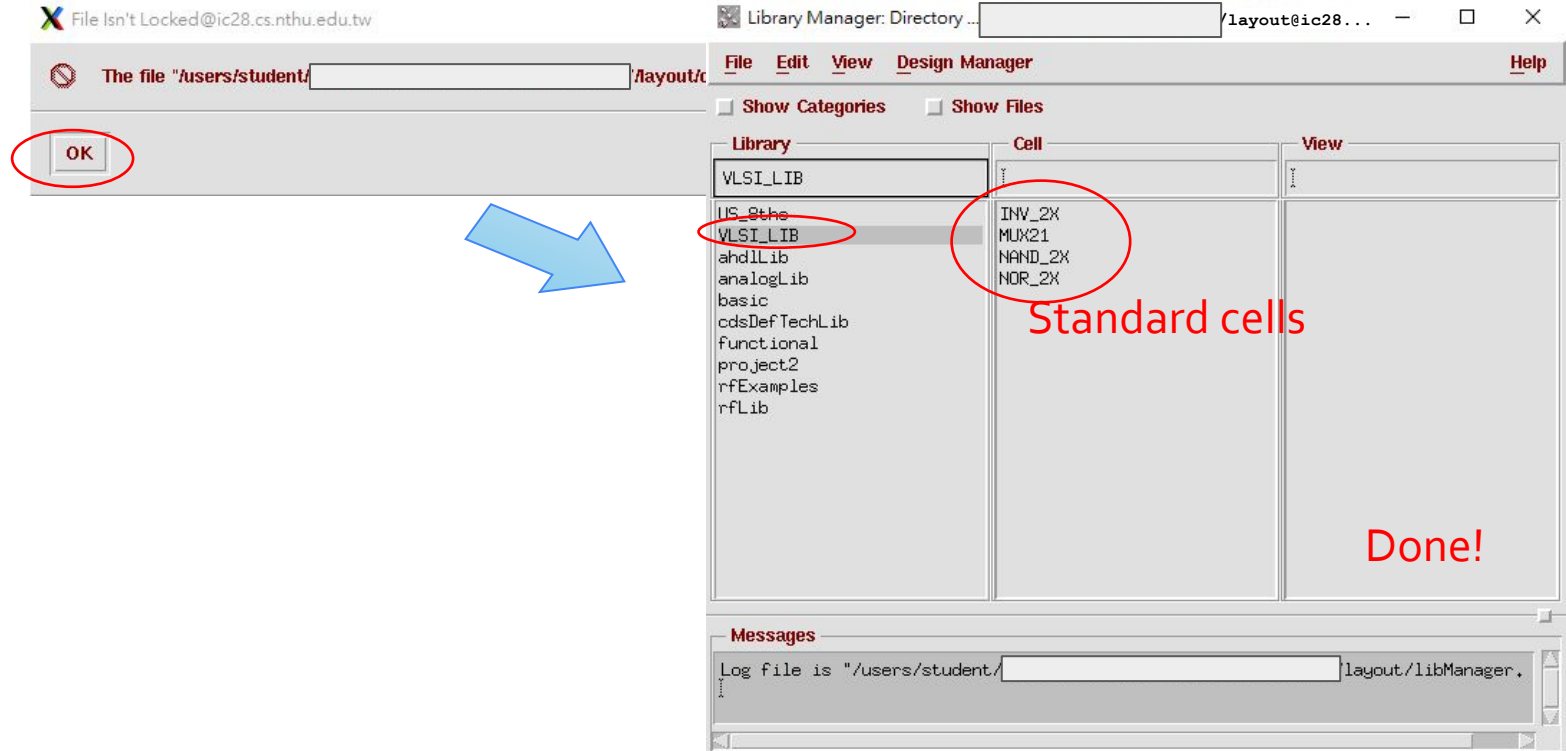


Outline

- Cell-Based Design
- Standard Cell Setting
- Cell Duplication for Logic Function
- Example
- Project
- Grading

Instance Creation (1)

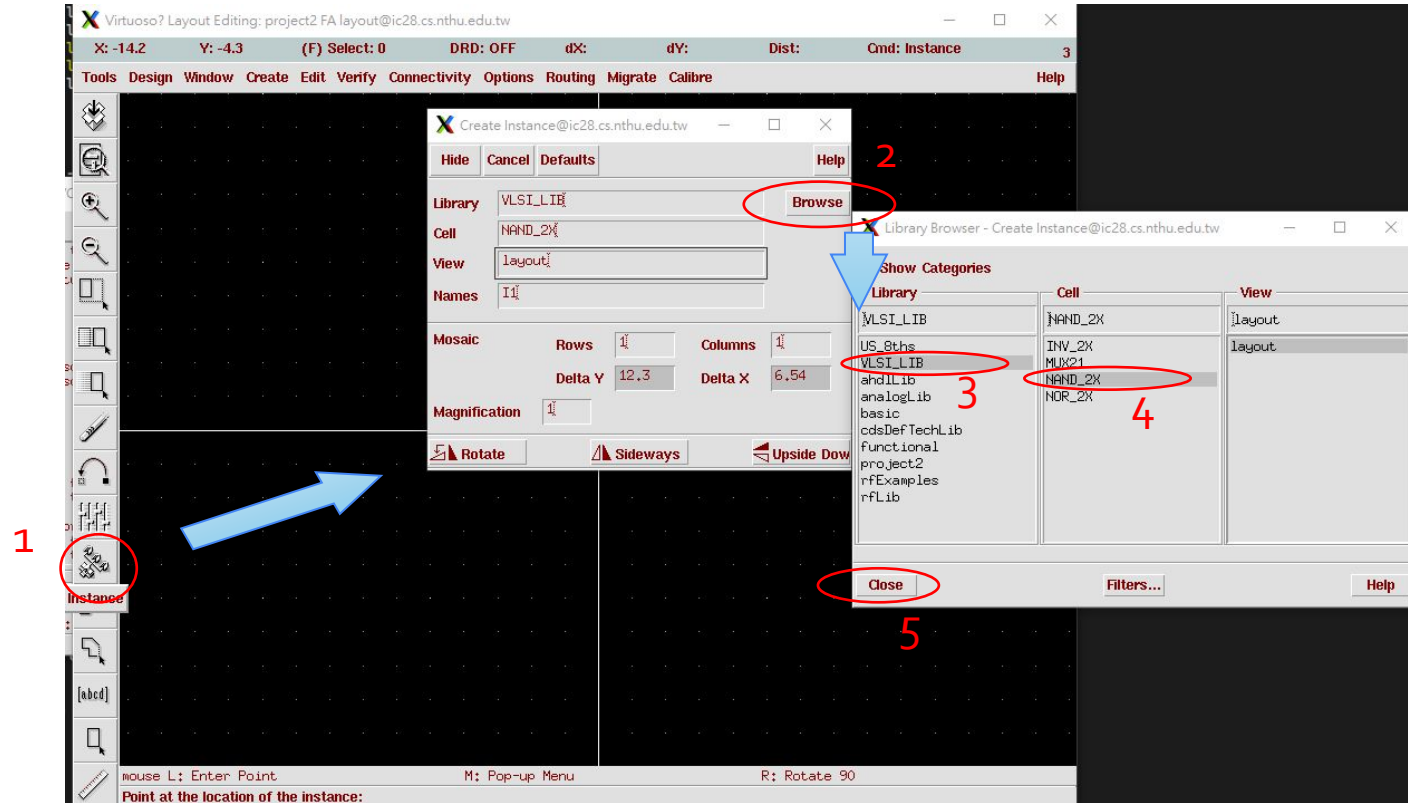


Instance Creation (2)

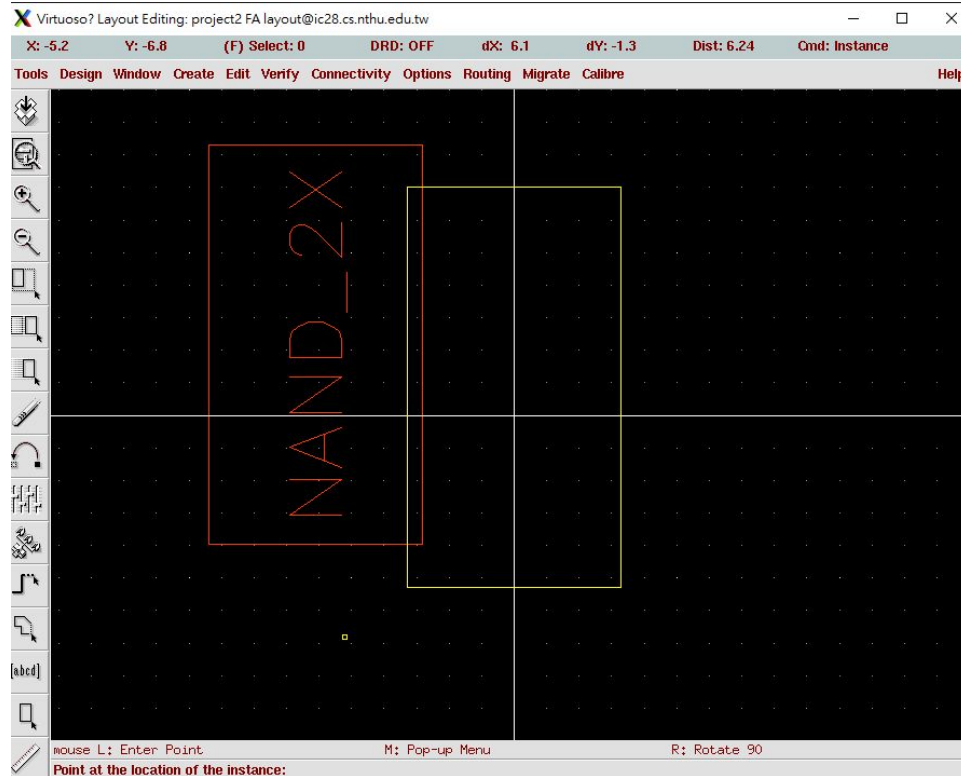


- Left click to place the cell.


Instance Creation (3)

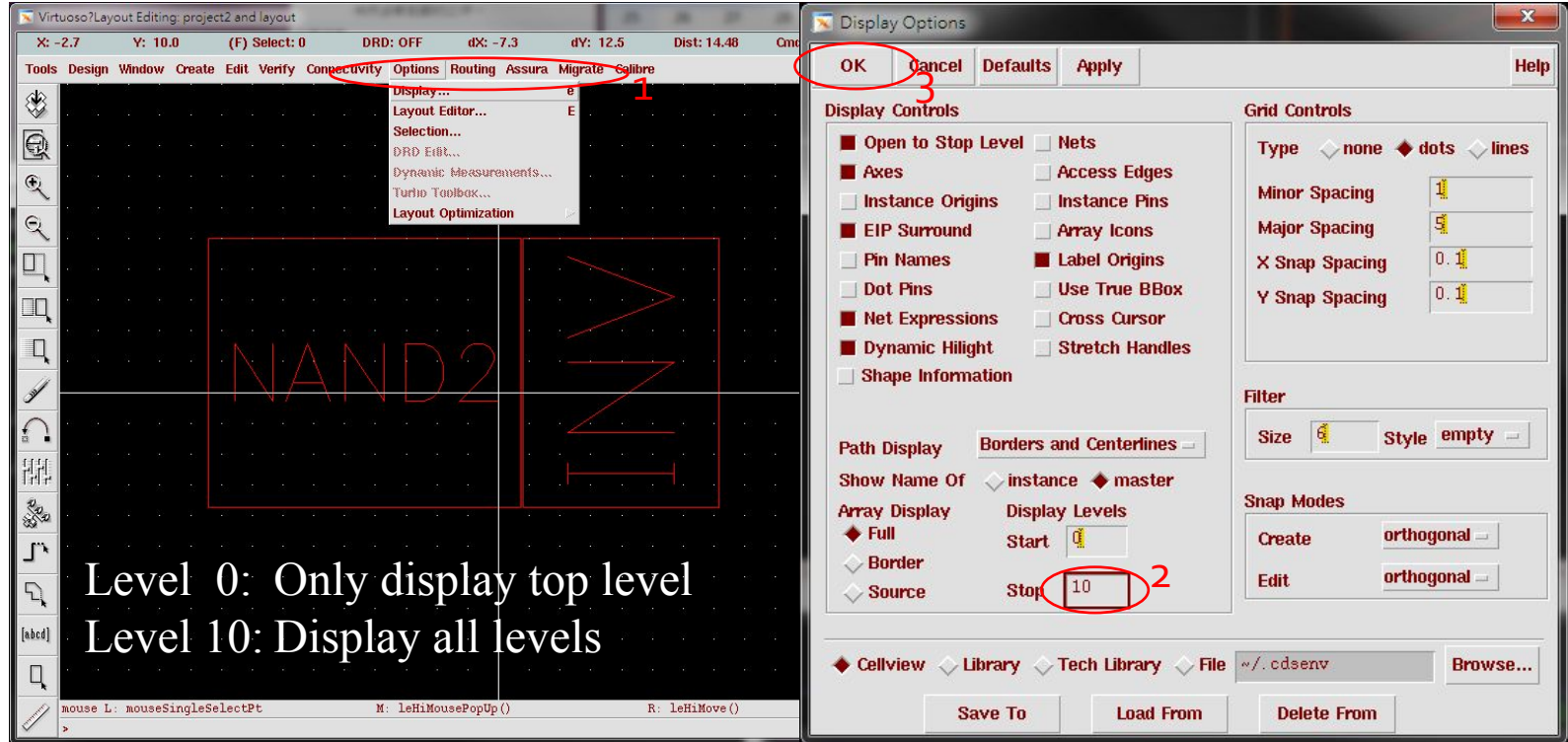

Instance Creation (4)

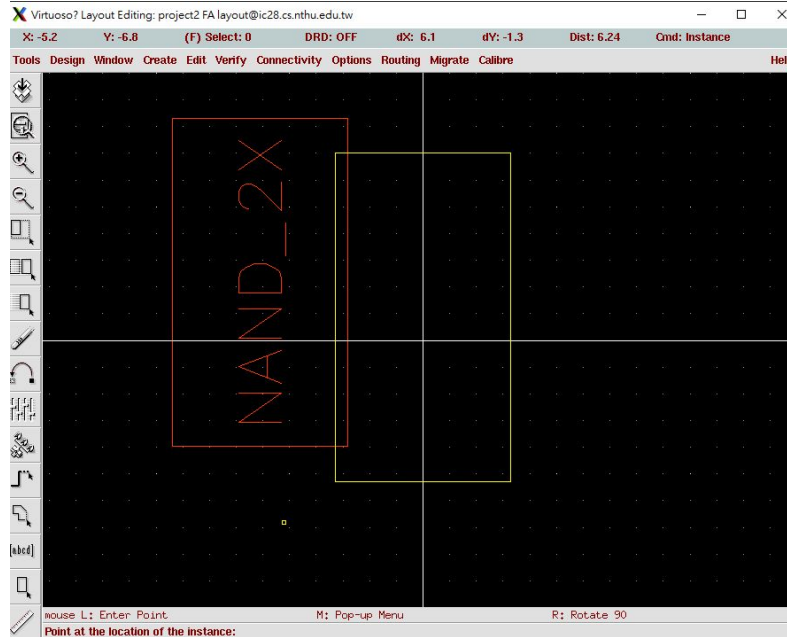

Display level 0

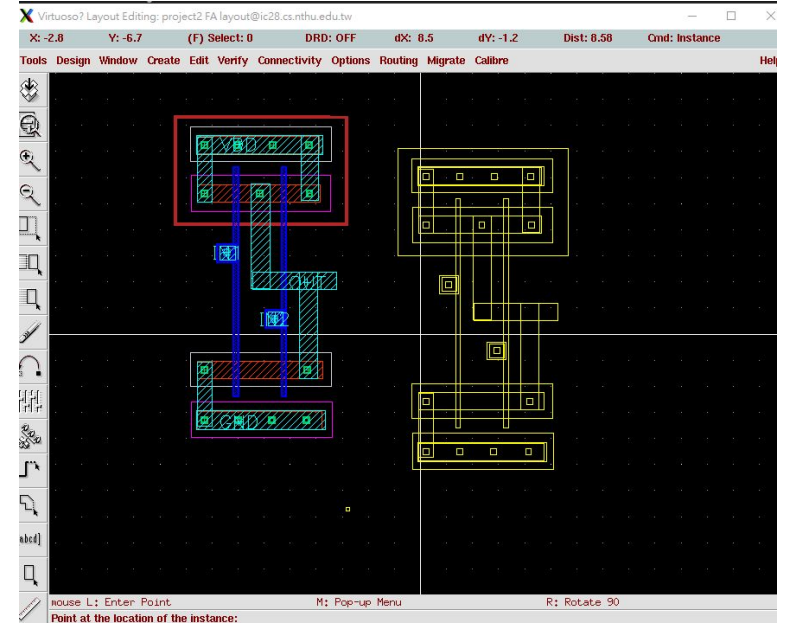

Display level 10

Hotkey - Display level

Cadence Virtuoso Layout Hotkeys


| | Category | Action | Hotkey |
|------------------|----------------|------------------------------------|---------|
| V I E W | ZOOM | IN | cntl+Z |
| | | OUT | shift+Z |
| | FIT | Fit whole layout to exiting window | f |
| | VIEW HIERARCHY | MORE DETAIL | shift+F |
| | | LESS DETAIL | cntl+f |
| | REDRAW | --- | cntl+r |
| E D I T | STRETCH | --- | s |
| | MOVE | --- | m |
| | COPY | --- | c |
| | UNDO | --- | u |
| | SELECT ALL | Select all objects on the window | cntl +a |
| | DESELECT ALL | Deselects all selected objects | cntl +d |
| M I S C | PROPERTIES | Show properties of selected object | q |
| | RULER | CREATE | k |
| | | DELETE ALL | shift+K |
| | HIERARCHY | DESCEND | shift+X |
| | | RETURN | shift+B |

Outline

- Cell-Based Design
- Standard Cell Setting
- Cell Duplication for Logic Function
- **Example**
- Project
- Grading


Example: $f = a * b * c * d \quad (1)$

Cell duplication

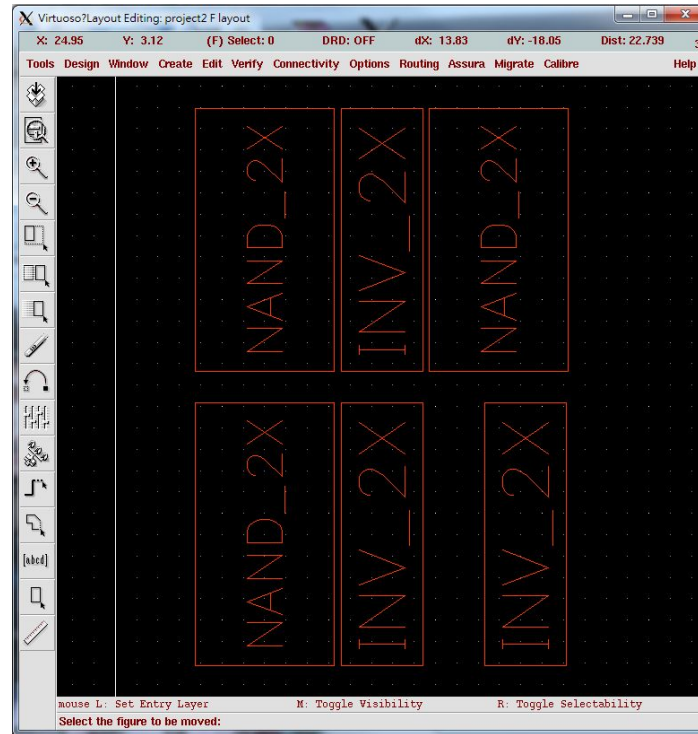


Example: $f = a * b * c * d$ (2)

Metal wire connection

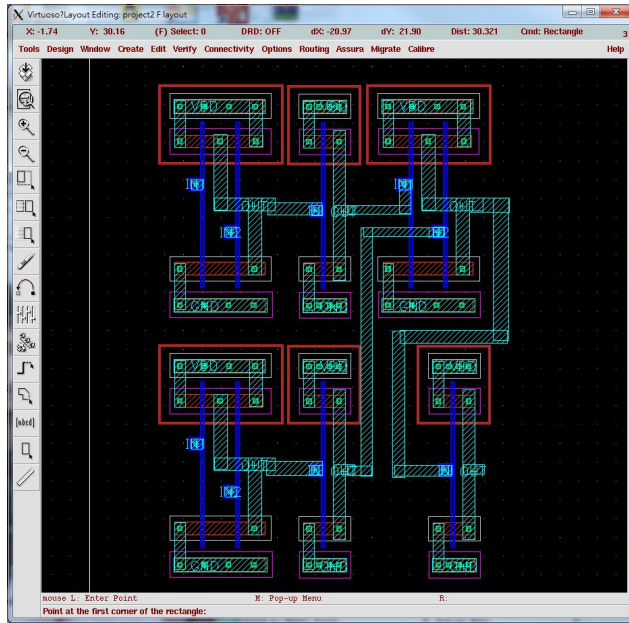


Display level 10

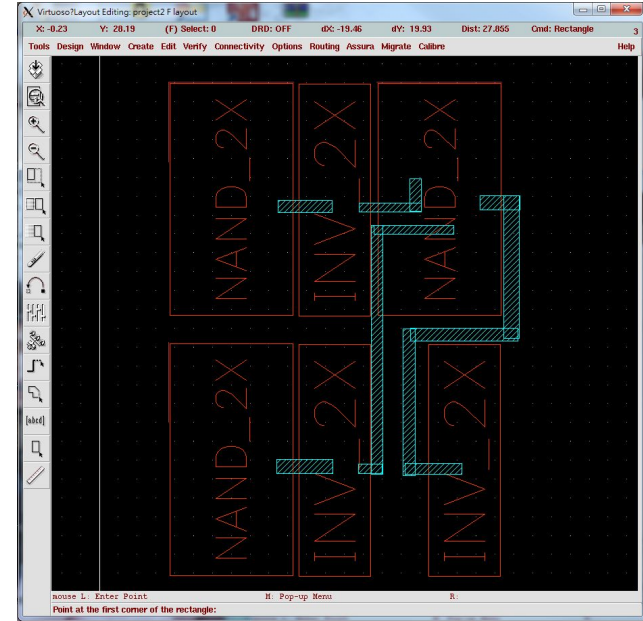


Display level 0

Example: $f = a * b * c * d$ (3)


Vdd / Gnd Connection **by metal 1**

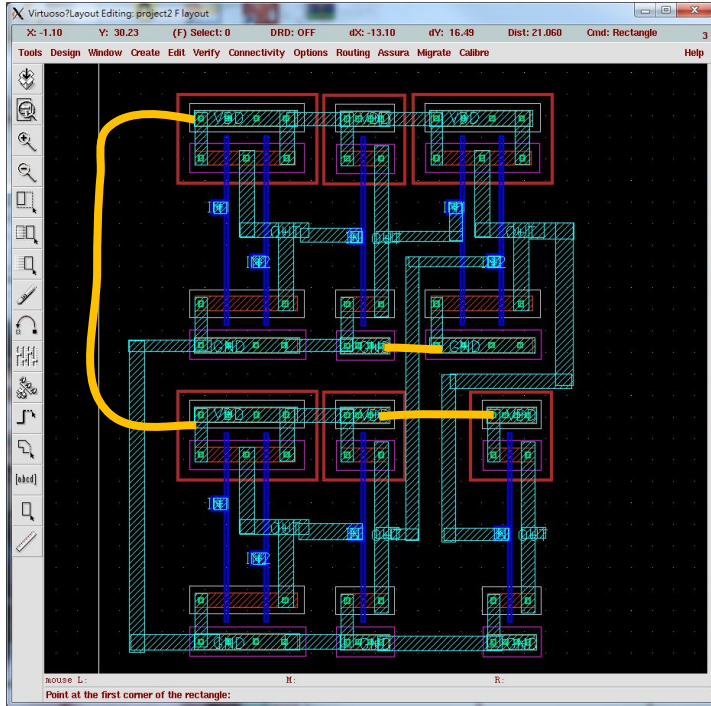

- You **cannot just** use metal 1 to connect these segments .
- It causes unexpected shorts to other metal 1!

Example: $f = a * b * c * d$ (4)


Vdd / Gnd Connection **by metal 2**

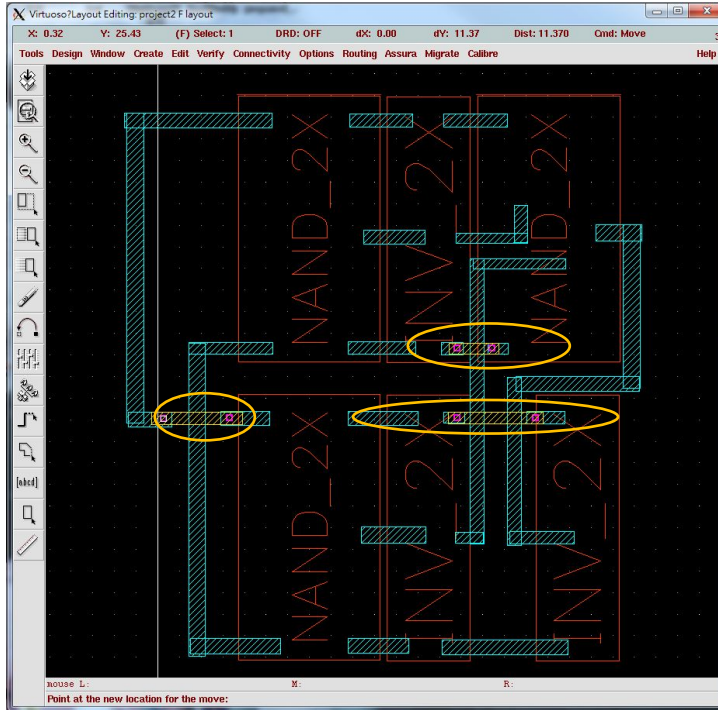



Example: $f = a * b * c * d$ (5)

Vdd / Gnd Connection **by metal 2**

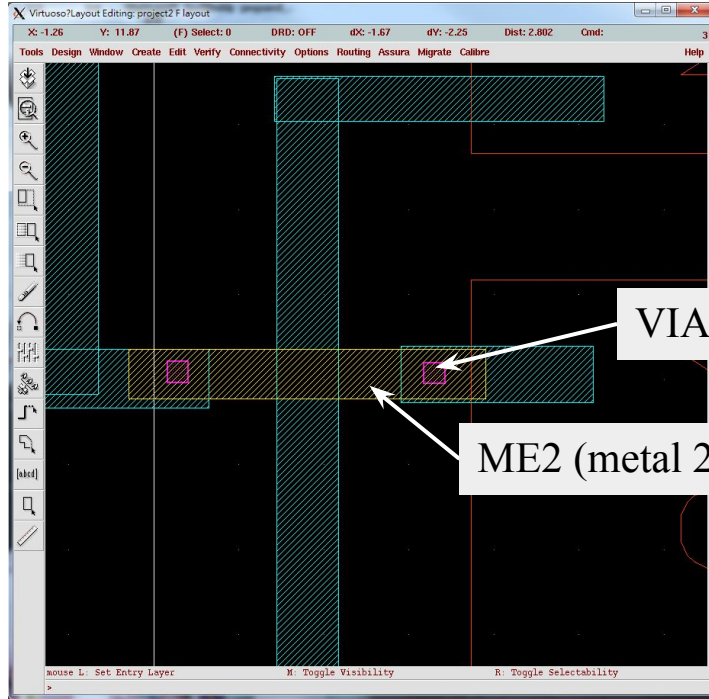


Size of VIA must be
 $0.25\mu\text{m} * 0.25\mu\text{m}$

VIA1


ME2 (metal 2)

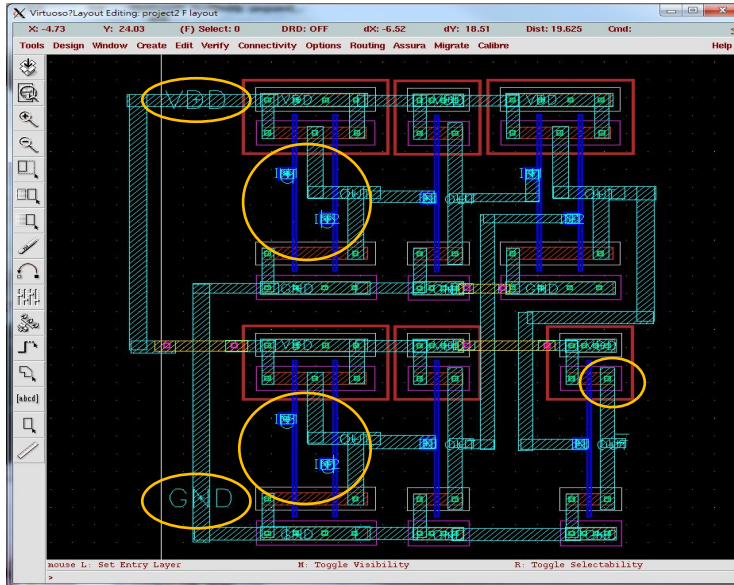Example: $f = a * b * c * d$ (6)

Labels in standard cells are different from current cell!
*P.S. You should display **level zero** for checking*



Display level 10

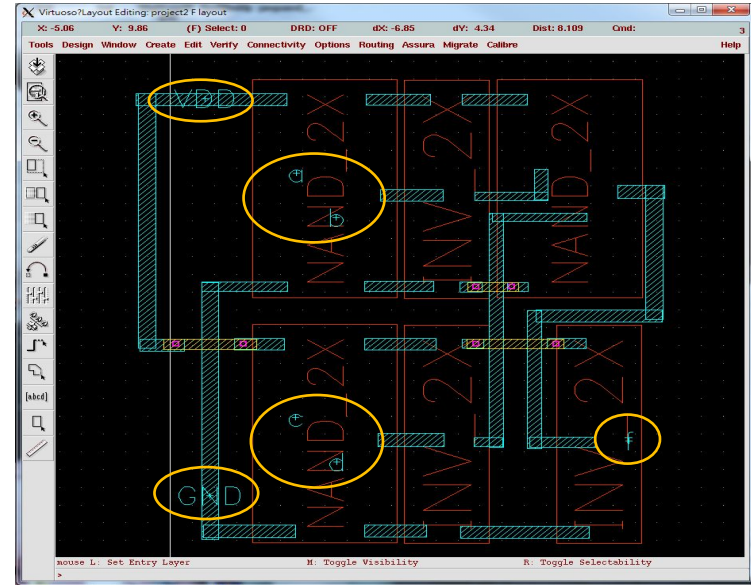


Display level 0


Another clearer example: $\text{out} = \text{in1} * \text{in2}$

Labels in standard cells are different from current cell!

 *P.S. You should display **level zero** for checking*



Display level 10

 

Display level 0

Example: $f = a * b * c * d$ (7)

- Schematic file “[ADDER3.src.net](#)”
- “x” represents the **cell (subcircuit call)**
 - x_[name_as_you_like] [Pin 1] [Pin 2] ... [Pin N] [Cell_type_name]
- E.g.

```
.subckt F a b c d f VDD GND
x_and1_nand a b abiOut VDD GND NAND_2X
x_and1_inv abiOut abOut VDD GND INV_2X
x_and2_nand c d cdiOut VDD GND NAND_2X
x_and2_inv cdiOut cdOut VDD GND INV_2X
x_and3_nand abOut cdOut fiOut VDD GND NAND_2X
x_and3_inv fiOut f VDD GND INV_2X
.ends
```

Example: $f = a * b * c * d$ (8)

- Definition of standard cells also needs to be put into schematic file.
- You can find standard definition at `VLSI_LIB/[Cell_name]`
 - E.g. `VLSI_LIB/NAND_2X/NAND2X.src.net`

```

nuthcad.cs.nthu.edu.tw - PuTTY
.subckt F a b c d f VDD GND
x_and1_nand      a          b          abiOut  VDD GND NAND_2X
x_and1_inv       abiOut     abOut      VDD GND INV_2X
x_and2_nand      c          d          cdiOut  VDD GND NAND_2X
x_and2_inv       cdiOut     cdOut      VDD GND INV_2X
x_and3_nand      abOut      cdOut      fiOut   VDD GND NAND_2X
x_and3_inv       fiOut     f          VDD GND INV_2X
.ends

.subckt INV_2X IN OUT VDD GND
mp1 OUT IN VDD VDD P_18 w=0.67u l=0.18u
mn1 OUT IN GND GND N_18 w=0.67u l=0.18u
.ends

.subckt NAND_2X IN1 IN2 OUT VDD GND
mp1 OUT IN1 VDD VDD P_18 w=0.67u l=0.18u
mp2 OUT IN2 VDD VDD P_18 w=0.67u l=0.18u
mn1 NET IN1 GND GND N_18 w=0.67u l=0.18u
mn2 OUT IN2 NET GND N_18 w=0.67u l=0.18u
.ends

-- INSERT --
21,1
Top

```

Outline

- Cell-Based Design
- Standard Cell Setting
- Cell Duplication for Logic Function
- Example
- **Project**
 - Step 1: 2x1 multiplexer
 - Step 2: 1-bit full adder
 - Step 3: 3-bit carry select adder
- Grading

Project Requirements

Step 1: Design a 2x1 multiplexer: MUX21 (already given in `VLSI_LIB`)

- Use **cell-based** design
- Pass DRC and LVS

Step 2: Design a 1-bit full adder: FA

- Use **cell-based** design
- Pass DRC and LVS

Step 3: Design a **3-bit carry select adder: ADDER3**

- Design a transistor-level schematic yourself
- Draw a **cell-based** layout (reuse your full_adder & MUX)
- Pass DRC and LVS

Step 1: 2x1 Multiplexer

- Cell name: **MUX21** (given in `VLSI_LIB`)

- Input


- in1
- in2
- ctrl

- Output

- out

- Function

 - $\text{out} = (\text{ctrl} == 0) ? \text{in1} : \text{in2}$



Step 2: 1-bit Full Adder

- Cell name: FA

- Input


- a
- b
- c_{in}

- Output

- c_{out}
- sum

- Function

- { c_{out} , sum } = a + b + c_{in}

 

| Inputs | | | Outputs | |
|--------|---|--------|---------|---------|
| A | B | C – IN | Sum | C – Out |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |



Step 3: 3-bit Carry Select Adder

- Cell name: ADDER3

- Input


- $A[0:2]$: A_0, A_1, A_2
- $B[0:2]$: B_0, B_1, B_2
- C_{in}

- Output

- $S[0:2]$: S_0, S_1, S_2
- C_{out}

- Function

 - $\{ C_{out}, S[0:2] \} = A[0:2] + B[0:2] + C_{in}$





Transistor Schematic

- Schematic format

- Cell and port name should be named as follows
- I/O port must be *in order*

```
.subckt ADDER3 A0 A1 A2 B0 B1 B2 CIN S0 S1 S2 COUT VDD GND
```

```
...
```

```
.ends
```

```
.subckt FA a b c_in sum c_out VDD GND
```

```
...
```

```
.ends
```

```
.subckt MUX21 in1 in2 ctrl out VDD GND
```

```
...
```

```
.ends
```

```
...
```



Layout

- Labels should be **STRICTLY** named as follows.
 - Cell name
 - ADDER3
 - Input
 - A0, A1, A2, B0, B1, B2, CIN, VDD, GND
 - Output
 - S0, S1, S2, COUT
 - No naming constraint to internal signals
 - You can use only **metal layer 1** and **2** (**ME1** & **ME2**)

Outline

- Cell-Based Design
- Standard Cell Setting
- Cell Duplication for Logic Function
- Example
- Project
- Grading



Report

- Your report should contain the following content, and you can add more as you wish.
 - Your **NAME** and **STUDENT ID**
 - **FIVE** screenclips:
 - Layout with rulers (**BOTH** display *level 10* and *level 0*)
 - DRC summary report
 - The message of passing LVS... ✓ [CORRECT] ☺
 - LVS schematic (the text file, ADDER3.src.net)
 - What else did you do to enhance your layout quality?
 - What have you learned from this homework? What problem(s) have you encountered in this homework?



Grading (1)

- Submission deadline: 2021/12/31 (Fri.) 23:59

- TWO files to upload:

1. A `.pdf` format report
2. A `.tar.gz` file includes all files in directory `layout`.

You can use the following command to compress your directory on a workstation:

```
$ tar -zcvf [Student_ID]_project2.tar.gz ./layout
```

(More compress & extraction commands: <http://note.drx.tw/2008/04/command.html>)

- Upload 1. and 2. to eeclass

- Name the files as “[StudentID]_report2.pdf” and “[StudentID]_project2.tar.gz”, respectively.


Grading (2)

- Score breakdown

- Layout Area 30% (以全班1/3、2/3為分界, 給予三等級分數)
- DRC pass 20%
- Layout 20%
- LVS schematic 20%
- Report 10%
- Uploading date
 - Early bird bonus: Extra 10 points for submission before 2021/12/24 (Fri.) 23:59
 - No late submission

Layout with Rulers to Show Area

 - No ruler: -10 points
- Ruler **must not be** too large or too small.





Notice

- File Naming
 - Library name: **project2**
 - Cell: **FA, ADDER3**
 - LVS netlist name: **ADDER3.src.net**
- Submission after deadline → **0 point**
- Plagiarism → **0 point**
- Dishonest contents in the report → **0 point**